Thapar Institute of Engineering and Technology, Patiala **Department of Electronics & Communication Engineering** Jan-June, 2021

Course: Engineering Design Project II (UTA014)

Submission guidelines of assignment-3A (ECED)

Assignment must be submitted by each student individually as per the following guidelines.

- The last date of submission is June 10, 2021. Submit your assignment-3A on LMS and Google form (circulated by respective faculty members) on or before the last date.
- A maximum weightage of this assignment is 10 marks.
- Assignment must be in **typed form** with neat diagrams (images) (2-3 pages only) and the student is required to submit a soft copy (pdf, up to 1 MB) of his/her assignment.
- Marks will be reduced if **not submitted** within **due date** of submission **without prior** permission.
- Assignment copied from other students will be treated as the case of plagiarism and marks will be **deducted** from the **entire copied version** (s) submitted by students.

Assignment-3A (ECED)

Objective:

Design a schematic diagram and it PCB layout for any one of the electronics circuits of your choice from the following list using **Autodesk Eagle** software.

- BJT Transistor amplifier: Common emitter (CE) or common Base (CB) or common collector (CC)
- **Diode full wave rectifier**: Center taped rectifier **or** Bridge rectifier
- **Diode clipper**: Positive clipper **or** Negative Clipper **or** Biased clipper
- **Diode clamper**: Positive clamper **or** Negative Clamper **or** Biased clamper
- Operational amplifier: Adder circuit or subtractor circuit or Differentiator circuit or integrator circuit

The project write-up **must include** the following points in detail:

- Basic description of electronics circuit diagram
- Schematic diagram of the electronic circuit through Autodesk Eagle
- PCB layout diagram of the electronic circuit through Autodesk Eagle
- Applications of the electronic circuit